
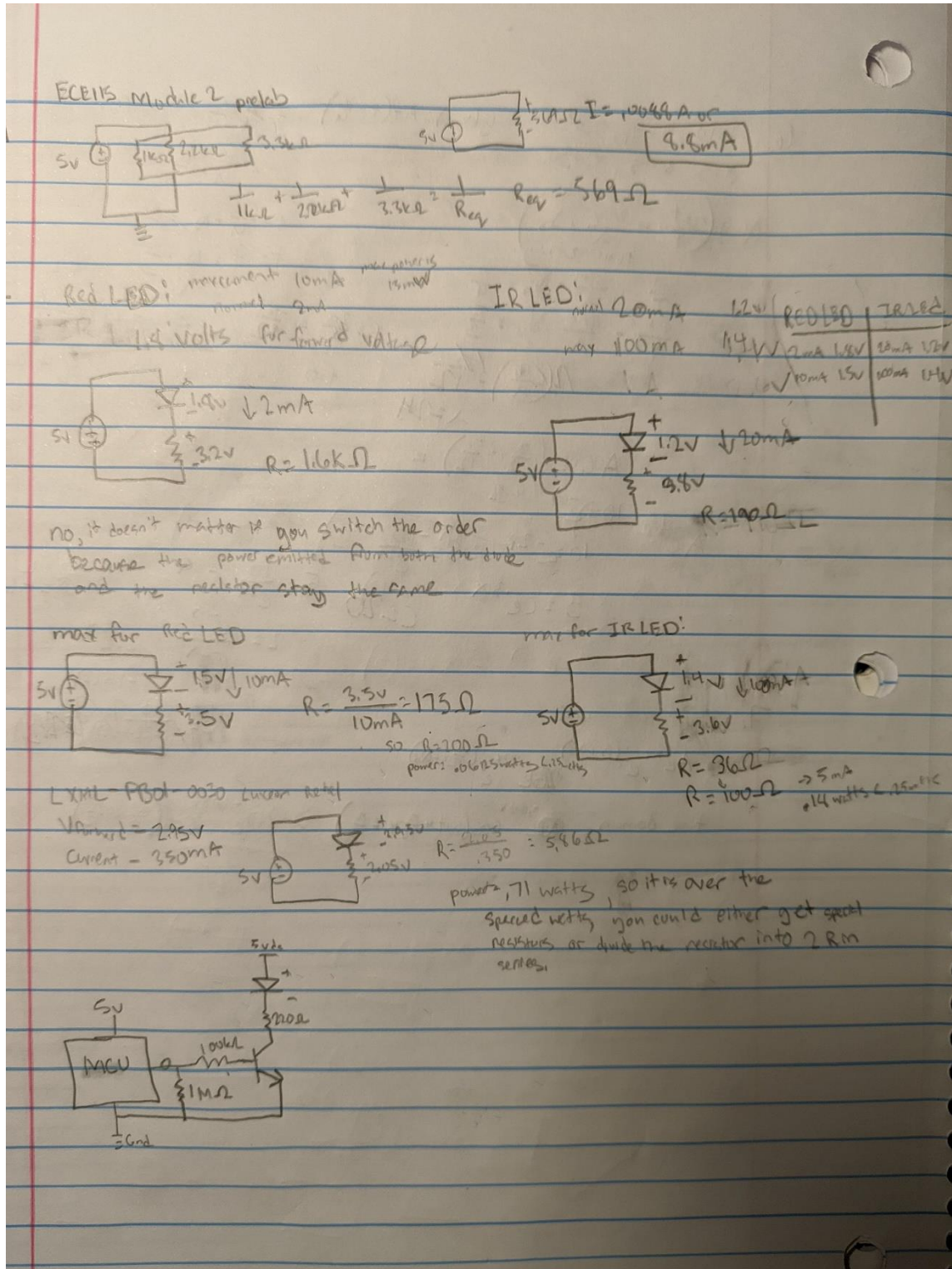


ECE 115 Module 2 Prelab

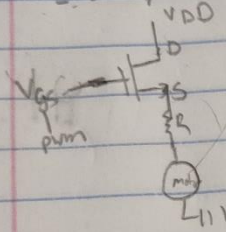

EE 115 Lab 2



b) by changing V_G to change the current through the motor

c) 2Amps

d) ~~no~~ For the motor because the max current is 23A
no for BJT because max current is 200mA